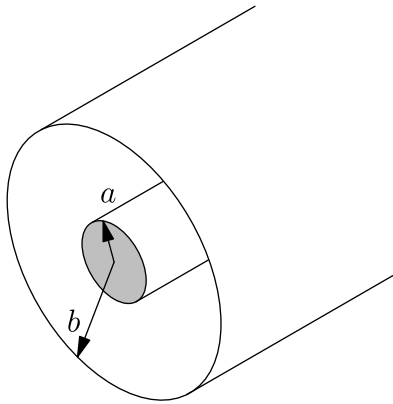


## J02E.1—Coaxial Transmission Line

### Problem

An infinitely long coaxial transmission line made from perfect conductors lies along the  $z$  axis, as shown below. The inner wire is of radius  $a$ , the outer wire is a cylinder of inner radius  $b$ , and the space between is filled with a material of (relative) dielectric constant  $\epsilon$  and (relative) permeability  $\mu$ .



- a) Find the speed  $v$  of the waves down the transmission line, the magnitude of the ratio  $E/B$  of the electric and magnetic fields, and the impedance  $Z = V(z, t)/I(z, t)$  of the transmission line where  $I(z, t)$  is the current in each of the wires and  $V(z, t)$  is the voltage difference between the two wires.

As on all parts of this exam, either MKSA or Gaussian units may be employed.

- b) A transmission line of impedance  $Z_1$  for  $z < 0$  is connected to a line of impedance  $Z_2$  for  $z > 0$ . A wave  $E_0 e^{i(kz - \omega t)}$  is incident from  $z = -\infty$ . Derive an expression for the amplitudes of the transmitted and reflected waves.
- c) Assume the answer to part a) for the impedance of the transmission line was  $Z$ . It is desired to split the signal from the transmission line into two identical lines as shown in the Figure. What value of  $R$  for the matching resistors will ensure that there are no reflections?

